

B.C.A Semester - 2 (CBCS) Examination**March/April- 2019 (Old Course)****CS-09 COMPUTER ORGANIZATION & ARCHITECTURE
(CORE)****Time: 2:30 Hours****Marks: 70****Instructions:**

1. All questions are compulsory.
 2. Figures to the right indicate marks.
-

Que-1 (A) Answer following Questions [04]

1. _____ and _____ Gates are known as Universal Gates.
2. _____ is a modified OR gate that produces a HIGH output when only one of the input is HIGH.
3. The combinational circuit that performs the arithmetic addition of two bits is called _____.
4. The _____ is an electronic circuit that gives a HIGH output (1) only if all its inputs are high

Que-1 (B) Answer Any One [02]

1. Explain OR Gate with truth table.
2. What is Boolean algebra?

Que-1 (C) Answer Any One [03]

1. Explain Half Adder.
2. Explain Sequential Circuit.

Que-1 (D) Answer Any One [05]

1. Write short note on JK Master-Slave Flip flop.
2. Write short note on Karnaugh map.

Que-2 (A) Answer following Questions [04]

1. A _____ is a combinational circuit that converts binary information from n coded inputs to a maximum of 2^n unique outputs.
2. A _____ is combinational circuit that selects binary information from one of many input lines and directs it to a single output line.
3. A _____ is a group of flip-flops capable of storing one bit of information.
4. A register capable of shifting its binary information in one or both directions is called a _____.

Que-2 (B) Answer Any One [02]

1. Write the application of the Multiplexer.
2. Explain Encoder.

Que-2 (C) Answer Any One [03]

1. Draw the block diagram of register
2. Explain binary counter

Que-2 (D) Answer Any One [05]

1. Construct 4-to-16 line decoder using our 2-to-4 line decoder
2. Explain parallel register and shift register.

Que-3 (A) Answer following Questions [04]

1. $11001 / 10 =$ _____
2. $1110 * 101 =$ _____
3. $11010 / 11 =$ _____
4. $1101 * 10 =$ _____

- Que-3 (B) Answer Any One [02]**
1. Explain rules of binary division.
2. Calculate : 1011.101×101.01
- Que-3 (C) Answer Any One [03]**
1. Explain fixed point representation.
2. Explain binary multiplication and binary division rules.
- Que-3 (D) Answer Any One [05]**
1. Explain parity bit with error detection code.
2. Explain floating point representation.
- Que-4 (A) Answer following Questions [04]**
1. The register that holds the address of the stack is called a _____ because its value always points at the top item in the stack.
2. The common arithmetic expressions are written in _____ with each operator written between the operands.
3. The _____ of computer system is the place where the actual execution of instruction takes place during the processing operation.
4. _____ is a signal send by external device to the processor to perform a task When the processor is currently performing a certain task.
- Que-4 (B) Answer Any One [02]**
1. Explain major component of CPU.
2. What is Control Word?
- Que-4 (C) Answer Any One [03]**
1. Write a note on register stack.
2. What is interrupt? Explain types of interrupts.
- Que-4 (D) Answer Any One [05]**
1. Discuss polish and reverse polish notation
2. Explain General Register Organization in Detail with Micro Operation?
- Que-5 (A) Answer following Questions [04]**
1. A collection of cables through which data is transferred to one peripheral device to another peripheral device is known as _____.
2. _____ is bi-directional bus which allows the transfer of data between the Microprocessor and memory or peripheral devices.
3. Full Form of DMA is _____.
4. _____ connects processor with main memory.
- Que-5 (B) Answer Any One [02]**
1. Explain following data transfer method of DMA.
a) Burst transfer b) Cycle stealing
2. Explain different I/O commands.
- Que-5 (C) Answer Any One [03]**
1. Explain Memory stack
2. Write short note on IOP
- Que-5 (D) Answer Any One [05]**
1. Write short note on DMA.
2. Write short note on I/O Interface.
