

B.Sc. Semester - 5 (Remedial) (CBCS) Examination**March/April-2024 (Old Course)****SOLID STATE ELECTRONICS (CORE)****Time: 2:30 Hours****Marks: 70****Instructions:**

1. All questions are compulsory.
2. Figures to the right indicate marks.

-
- Que-1(A) Answer the following question (any one). (07)
- (1) Write a note on transformer coupled amplifier.
 - (2) Explain in brief: push-pull amplifier.
- Que-1(B) Answer the following question (any one). (04)
- (1) Write a note on direct coupled amplifier.
 - (2) Explain class A power amplifier.
- Que-1(C) Answer the following question (any three). (03)
- (1) Unit of voltage gain is
 - (2) coupled amplifier has poor frequency response.
 - (3) For extremely low frequency signal amplification coupled amplifier is used.
 - (4) The change of output wave shape from the input wave shape of amplifier is known as
 - (5) If the collector current flows for less than half cycle of the input signal, it is called class power amplifier.
- Que-2(A) Answer the *following* question (any one). (07)
- (1) write a note on bistable multivibrators.
 - (2) Write a note on monostable multivibrators.
- Que-2(B) Answer the following question (any one). (04)
- (1) Write a short note on switching action of transistor.
 - (2) Explain biased positive clipper.
- Que-2(C) Answer the following question (any three). (03)
- (1) switch has very fast operating speed.
 - (2) A multivibrator is an electronic circuit with feedback.
 - (3) Astable multivibrator has stable states.
 - (4) Bistable multivibrator is also known as
 - (5) A negative clipper removes half cycle of the input signal.
- Que-3(A) Answer the following question (any one). (07)
- (1) Explain regulated power supply.
 - (2) Explain functioning of an OP-AMP as a linear amplifier.
- Que-3(B) Answer the following question (any one). (04)
- (1) Write a short note on ordinary d.c. power supply.
 - (2) Explain differentiator.

- Que-3(C) Answer the following question (any three). (03)
- (1) In an unregulated power supply, if load current increase, the output votage
 - (2) A zener diode utilises characteristics for voltage regulation.
 - (3) Full form of IC is
 - (4) ICs have poor isolation between components.
 - (5) Full form of OP-AMP is
- Que-4(A) Answer the following question (any one). (07)
- (1) Explain self generating inductive transducers.
 - (2) Write a note on strain gauge.
- Que-4(B) Answer the following question (any one). (04)
- (1) Explain resistive position transducer.
 - (2) Write a short note on capacitive pressure transducer.
- Que-4(C) Answer the following question (any three). (03)
- (1) is device which converts energy from one form to another form.
 - (2) Thermistor is type of transducer.
 - (3) Thermistor has temperature co-efficient.
 - (4) Photoconductive cell is also known as
 - (5) Microphone convers an acoustic energy into an energy.
- Que-5(A) Answer the following question (any one). (07)
- (1) Write a note on DVM.
 - (2) Explain R-S flip-flop.
- Que-5(B) Answer the following question (any one). (04)
- (1) Explain essentials of an electronic instruments.
 - (2) Write a short note on demultiplexer.
- Que-5(C) Answer the following question (any three). (03)
- (1) A is a measuring instrument which can measure voltage, current and resistance.
 - (2) Full form of CRO is
 - (3) A is a circuit which has one input and number of outputs.
 - (4) flip flop has only one input.
 - (5) flip flop can be used to build counter.
