

B.Sc. Semester - 6 (CBCS) Examination
March/April-2024 (NEW COURSE)
Solid State Electronics (Core (New))

Time: 2:30 Hours**Marks: 70****Instructions:**

1. All questions are compulsory.
2. Figures to the right indicate marks.

-
- Que.1(A) Answer the following question. (any two) (10)
- (1) Write a note on transformer coupled amplifier.
 - (2) Explain performance quantities of power amplifiers.
 - (3) Explain push-pull amplifier.
- Que.1(B) Answer the following question (any one) (04)
- (1) Write a short note on role of capacitors in multistage transistor amplifier.
 - (2) Explain the difference between a voltage and a power amplifier.
- Que.2(A) Answer the following question. (any two) (10)
- (1) Explain switching action of transistor.
 - (2) Write a note on monostable multivibrator.
 - (3) Explain integrating circuit.
- Que.2(B) Answer the following question (any one) (04)
- (1) Explain positive clipper.
 - (2) Explain negative clamper.
- Que.3(A) Answer the following question. (any two) (10)
- (1) Explain transistor series voltage regulator.
 - (2) Explain Zener diode as a voltage regulator.
 - (3) Write a note on ICs with advantages and disadvantages.
- Que.3(B) Answer the following question (any one) (04)
- (1) If the d.c.output voltage is 400 V with no load attached to power supply but decreases to 300 V at full load, find the percentage voltage regulation.
 - (2) Give the comparisons between different types of ICs.
- Que.4(A) Answer the following question. (any two) (10)
- (1) Draw the basic circuit of differential amplifier and write its important points.
 - (2) Explain inverting amplifier.
 - (3) Discuss how an OP-Amp can be used as an Adder.
- Que.4(B) Answer the following question (any one) (04)
- (1) Write a note on OP-Amp as an integrator.
 - (2) Determine the voltage gain of a non-inverting OP-AMP amplifier having $R_1=100K$ and $R_f=1M\Omega$.
- Que.5(A) Answer the following question. (any two) (10)
- (1) Write note on digital voltmeter.
 - (2) Explain 16 to 1 multiplexer.
 - (3) Write a note on clocked RS flip-flop.
- Que.5(B) Answer the following question (any one) (04)
- (1) Write applications of CRO.
 - (2) Explain D flip-flop.
